

## Experiment No. 03

### 3.1 Experiment Name

Measurement and analysis of the gain in an instrumentation amplifier circuit

### 3.2 Objectives

- To observe the amplification of differential input and rejection of common-mode input
- To understand the basic principles and operation of an instrumentation amplifier
- To measure the differential gain in instrumentation amplifier

### 3.3 Theory

Instrumentation amplifiers are a specialized type of differential amplifier boasting exceptional common-mode rejection and high differential gain. Essentially, they amplify the difference between two input signals while simultaneously rejecting any common noise present in both.

This remarkable ability is achieved through a specific internal circuit configuration where a current,  $I_3$ , flows through resistors  $R_1$ ,  $R_2$ , and  $R_3$  based solely on the difference in voltage between the two inputs,  $V_{i1}$  and  $V_{i2}$ . As a result, the output voltage differential,  $V_{o1}-V_{o2}$ , becomes directly proportional to this voltage difference, further amplified by a factor of  $(1+2(R_1/R_3))$  and multiplied by the gain of the output stage ( $R_6/R_4$ ).

This clever design allows the instrumentation amplifier to effectively extract the desired signal while ignoring any unwanted common-mode noise, making it a valuable tool in various applications requiring precise and accurate measurements.

### 3.4 Apparatus

- ❖ Multimeter
- ❖ Oscilloscope
- ❖ Resistor
- ❖ Potentiometer
- ❖ Op-amp
- ❖ Project Board
- ❖ Wires
- ❖ Signal generator

### 3.5 Data Table (Measured value)

| $V_{i1}$ (volt) (p-p) | $V_{i2}$ (volt) (p-p) | $R_3$ ( $\Omega$ ) | $V_o$ (volt) | Differential gain,<br>$A_d = V_o/(V_{i1}-V_{i2})$ |
|-----------------------|-----------------------|--------------------|--------------|---|
| 4                     | 4.5                   | 10k                | 3            | 6   |
| 4                     | 4.5                   | 20k                | 2.8          | 5.6   |
| 4                     | 4.5                   | 40k                | 2.72         | 5.44  |
| 4                     | 4.5                   | infinity           | 0.5          | 1   |

### 3.6 Calculated value

For  $R_3 = 10k\Omega$ ;  $V_{i1} = 4$  V;  $V_{i2} = 4.5$  V

$$V_o = (1+2(10/10)) (10/10) (4-4.5) = 1.5 \text{ V}$$

$$A_d = V_o / V_{i1}-V_{i2} = 1.5/ 0.5 = 3$$

For  $R_3 = 20k\Omega$ ;  $V_{i1} = 4$  V;  $V_{i2} = 4.5$  V

$$V_o = (1+2(10/10)) (10/10) (4-4.5) = 1 \text{ V}$$

$$A_d = V_o / V_{i1} - V_{i2} = 1 / 0.5 = 2$$

For  $R_3 = 40\text{k}\Omega$ ;  $V_{i1} = 4\text{ V}$ ;  $V_{i2} = 4.5\text{ V}$

$$V_o = (1 + 2(10 / 40)) (10 / 10) (4 - 4.5) = 0.75\text{ V}$$

$$A_d = V_o / V_{i1} - V_{i2} = 0.75 / 0.5 = 1.5$$

For  $R_3 = \infty$ ;  $V_{i1} = 4\text{ V}$ ;  $V_{i2} = 4.5\text{ V}$

$$V_o = (1 + 2(10 / \infty)) (10 / 10) (4 - 4.5) = 0.5\text{ V}$$

$$A_d = V_o / V_{i1} - V_{i2} = 0.5 / 0.5 = 1$$

### 3.7 Discussion & Conclusion

The experiment successfully constructed the instrumentation circuit and accurately utilized a potentiometer as the gain resistor ( $R_3$ ). By varying the value of  $R_3$ , different differential gains ( $A_d$ ) were achieved, demonstrating its role in amplifying the differential input. While some discrepancies existed between the estimated and measured output, the observed decrease in  $A_d$  with increasing  $R_3$  aligned perfectly with theoretical predictions, validating the experiment's successful execution.