

PROJECT WORK

❖ Project Title

Design and implementation of an induction motor drive system using Arduino Uno and single-phase H-Bridge inverter.

❖ Objectives

- To get a better understanding of single-phase H-bridge inverter
- To understand the designing process of single-phase H-bridge inverter
- To get familiar with the practical implication of single-phase H-bridge inverter along with Arduino UNO

❖ Apparatus

Driver A3120 Optocoupler (2 pcs)	LED (2 pcs)
MOSFET IRF 240N (2 pcs)	Diode (2 pcs)
Two pin connector (2 pcs)	Capacitor (100 μ F; 2 pcs)
Three pin connector (2 pcs)	Resistor (1k Ω 4 pcs; 470 Ω 2pcs)
8 pin IC holder (2 pcs)	Flexible wire

❖ Experimental connection



Fig. 1: Experimental connection

❖ Arduino Code

```
int angle =0;
int dr=10;
void setup()
{
  pinMode(11, OUTPUT); // Timer 2
  pinMode(3, OUTPUT); // Timer 2
  TCCR2A = B10110001;
  TCCR2B = B00000101;
  TIMSK2 = B00000001;
}
ISR(TIMER2_OVF_vect)
{
  int duty = (255*sin(angle*3.1416/180)+255)/2;
  OCR2A = duty;
  if (duty==0){
    dr=0;
  }else{
    dr=10;
  }
  int y= duty+dr;
```

```

    if (y>=255){
        y=255;
    }
    else{
        y=y;
    }
    OCR2B=y;
    angle = angle +5;
    if (angle >360)
    {
        angle =0;
    }
}
void loop()
{
}

```

❖ Waveform

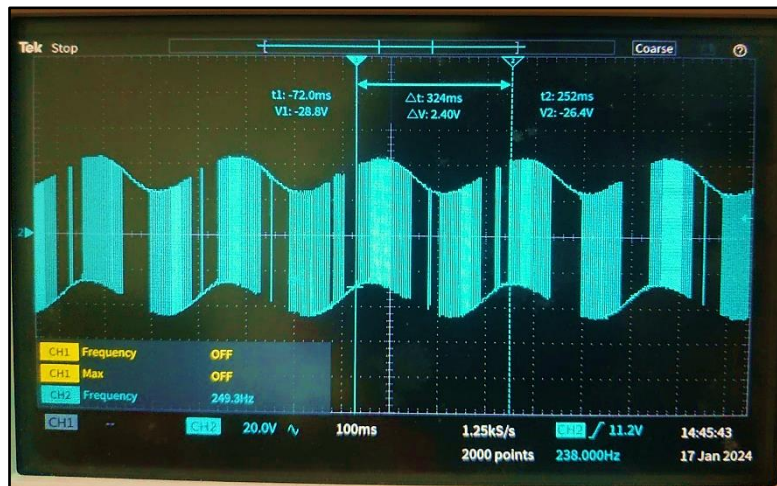


Fig. 2: The output waveform of induction motor

❖ Discussion & Conclusion

In this experiment, we successfully carried out the design and implementation of single-phase H-bridge inverter using an Arduino Uno. Our approach involved meticulous programming of the Arduino Uno to align with the project requirements. The induction motor, originally rated at 110V AC, exhibited an RMS voltage significantly below its rated voltage. To initiate motor activation, we adjusted the frequency accordingly. Thus, the induction motor operates at a lower frequency than its rating when the voltage falls below the rated frequency. Thus, the desired project output was obtained.